

## COMS10015 lab. worksheet #8


Although some questions have a written solution below, for others it will be more useful to experiment in a hands-on manner (e.g., using a concrete implementation). The file

[https://assets.phoo.org/COMS10015\\_2024\\_TB-4/csdsp/sheet/lab-08\\_s.tar.gz](https://assets.phoo.org/COMS10015_2024_TB-4/csdsp/sheet/lab-08_s.tar.gz)

supports such cases.

### §1. C-class, or core questions

- ▷ **S1[C]**. First we need to take stock of the problem itself: there is basically one input (the emergency stop button, denoted  $rst$ ) and six outputs (the traffic light values, denoted  $M_g, M_a$  and  $M_r$  for the main road and  $A_g, A_a$  and  $A_r$  for the access road). We *know* that Figure 1 can act as a starting point, in the sense that we just need to fill in each block with a problem-specific implementation.

 

**Figure 1:** Two generic FSM frameworks (for different clocking strategies) into which one can place implementations of the state,  $\delta$  (the transition function) and  $\omega$  (the output function).

Next we try to develop a precise description of the FSM behaviour. We need 7 states in total:  $S_0, S_1, \dots, S_5$  represent steps in the normal traffic light sequence, and  $S_6$  represents an extra emergency stop state. Figure 2 shows both a tabular and diagrammatic description of the transition function; in essence, it is similar to the counter example (in the sense that it cycles from  $S_0$  through to  $S_5$  and back again) if  $rst = 0$ , but if  $rst = 1$  in *any* state then we move to the  $S_6$ . As an aside, however, it is vital to view this description is *one* among several derived from what is (by design) a rather imprecise question. Put another way, we have made several assumptions and/or decisions. One example is the decision to use a separate emergency stop state, and have the FSM enter this as the next state of *any* current state if  $rst = 1$ ; the red lights are both forced on as a result of being in the emergency stop state, therefore, rather than by  $rst$  per se. Another valid approach might be to have  $\omega$  depend on  $rst$  as well (rather than only  $Q$ , turning it from a Moore-based into a Mealy-based FSM) and forcing the red lights on as soon as  $rst = 1$  irrespective of what state the FSM is in. This is arguably more attractive, in the sense that now the emergency stop is instant: we no longer need to wait for the next clock cycle when the next state is latched. Likewise, we have opted to make the first state listed in the question (i.e., **green** on the main road and **red** on the access road) the initial state; since the sequence is cyclic this decision seems a little arbitrary, so other options (plus what state the FSM restarts in after an emergency stop) might also seem reasonable.

Accepting the above, however, we next follow standard practice by translating the description into an implementation. Since  $2^3 = 8 > 7$  we can represent the current and next states via 3-bit integers  $Q = \langle Q_0, Q_1, Q_2 \rangle$  and

$Q' = \langle Q'_0, Q'_1, Q'_2 \rangle$  where

$$\begin{aligned} S_0 &\mapsto \langle 0, 0, 0 \rangle \equiv 000_{(2)} \\ S_1 &\mapsto \langle 1, 0, 0 \rangle \equiv 001_{(2)} \\ S_2 &\mapsto \langle 0, 1, 0 \rangle \equiv 010_{(2)} \\ S_3 &\mapsto \langle 1, 1, 0 \rangle \equiv 011_{(2)} \\ S_4 &\mapsto \langle 0, 0, 1 \rangle \equiv 100_{(2)} \\ S_5 &\mapsto \langle 1, 0, 1 \rangle \equiv 101_{(2)} \\ S_6 &\mapsto \langle 0, 1, 1 \rangle \equiv 110_{(2)} \end{aligned}$$


and we have one unused state (namely  $S_7 \mapsto \langle 1, 1, 1 \rangle$ ). As a result, the input and output registers can each be implemented by using three 1-bit storage components, i.e., either D-type latches or flip-flops.

Now we have a concrete value for each abstract state label, we can expand the tabular description of the FSM into a (lengthy) truth table:

				$\delta$			$\omega$					
$rst$	$Q_2$	$Q_1$	$Q_0$	$Q'_2$	$Q'_1$	$Q'_0$	$M_g$	$M_a$	$M_r$	$A_g$	$A_a$	$A_r$
0	0	0	0	0	0	1	1	0	0	0	0	1
0	0	0	1	0	1	0	0	1	0	0	0	1
0	0	1	0	0	1	1	0	0	1	0	1	0
0	0	1	1	1	0	0	0	0	1	1	0	0
0	1	0	0	1	0	1	0	0	1	0	1	0
0	1	0	1	0	0	0	0	1	0	0	0	1
0	1	1	0	0	0	0	0	0	1	0	0	1
0	1	1	1	?	?	?	?	?	?	?	?	?
1	0	0	0	1	1	0	1	0	0	0	0	1
1	0	0	1	1	1	0	0	1	0	0	0	1
1	0	1	0	1	1	0	0	0	1	0	1	0
1	0	1	1	1	1	0	0	0	1	1	0	0
1	1	0	0	1	1	0	0	0	1	0	1	0
1	1	0	1	1	1	0	0	1	0	0	0	1
1	1	1	0	1	1	0	0	0	1	0	0	1
1	1	1	1	?	?	?	?	?	?	?	?	?

Although this *looks* intimidating, we can use decomposition to consider the transition function and the output function *and* then each output signal within them separately:

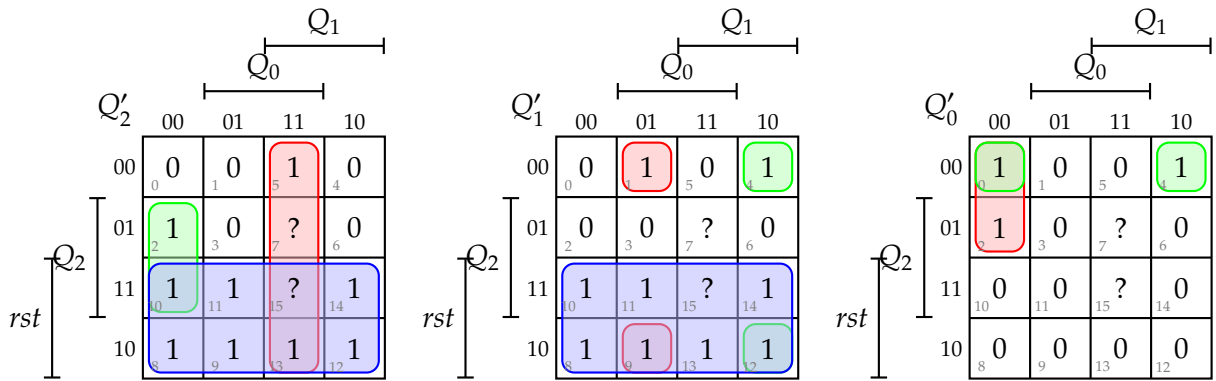- The transition function  $\delta$  is just three Boolean expressions, one for each  $Q'_i$ , using  $rst$ ,  $Q_2$ ,  $Q_1$  and  $Q_0$  as input. The Karnaugh maps



can be used to produce said expressions:


$$Q'_2 = (rst \wedge Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \vee (rst \wedge Q_2 \wedge Q_1 \wedge Q_0)$$

$$Q'_1 = (rst \wedge \neg Q_2 \wedge \neg Q_1 \wedge Q_0) \vee (rst \wedge \neg Q_2 \wedge Q_1 \wedge \neg Q_0)$$

$$Q'_0 = (\neg rst \wedge \neg Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \vee (\neg rst \wedge \neg Q_2 \wedge Q_1 \wedge \neg Q_0)$$

Q	$\delta$		$\omega$					
	$Q'$		$M_g$	$M_a$	$M_r$	$A_g$	$A_a$	$A_r$
	$rst = 0$	$rst = 1$						
$S_0$	$S_1$	$S_6$	1	0	0	0	0	1
$S_1$	$S_2$	$S_6$	0	1	0	0	0	1
$S_2$	$S_3$	$S_6$	0	0	1	0	1	0
$S_3$	$S_4$	$S_6$	0	0	1	1	0	0
$S_4$	$S_5$	$S_6$	0	0	1	0	1	0
$S_5$	$S_0$	$S_6$	0	1	0	0	0	1
$S_6$	$S_0$	$S_6$	0	0	1	0	0	1


(a) A tabular description.

 

(b) A diagrammatic description.

**Figure 2:** An FSM for the traffic light controller.

 - The output function  $\omega$  is just six Boolean expressions, one for each  $M_i$  and  $A_j$ , using  $rst$ ,  $Q_2$ ,  $Q_1$  and  $Q_0$  as input. The Karnaugh maps



can be used to produce said expressions:

$$\begin{aligned}
 M_g &= (\neg Q_2 \wedge \neg Q_1 \wedge \neg Q_0) & A_g &= (Q_1 \wedge Q_0) \\
 M_a &= (\neg Q_1 \wedge Q_0) & A_a &= (\neg Q_2 \wedge Q_1 \wedge \neg Q_0) \vee (Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \\
 M_r &= (Q_1) \vee (Q_2 \wedge \neg Q_0) & A_r &= (\neg Q_2 \wedge \neg Q_1) \vee (\neg Q_1 \wedge Q_0) \vee (Q_2 \wedge Q_1)
 \end{aligned}$$

The final step is to implement everything in LogisimEvo. Although this requires some effort, conceptually it means completing Figure 1 with 1) instantiations of the input and output registers, plus 2) instantiations of  $\delta$  and  $\omega$ , i.e., a translation of each expression into corresponding logic gates.

## §2. R-class, or revision questions

- ▷ **S2[R].** There is a set of solutions available at

[https://assets.phoo.org/COMS10015\\_2024\\_TB-4/csdsp/sheet/misc-revision\\_s.pdf](https://assets.phoo.org/COMS10015_2024_TB-4/csdsp/sheet/misc-revision_s.pdf)

### §3. A-class, or additional questions

- ▷ **S3[A].** There is no associated solution for this question, because it is somewhat open-ended with respect to 1) the goal or challenge presented, and/or 2) the assumptions and decisions you make, and therefore the design space of viable solutions.