COMS10015 quick(ish) reference hand-out: transistors and logic gates

Definition: informal

N-MOSFET :
$$g = V_{dd} = 5V \Rightarrow \text{ transistor is activated, } s \text{ and } d \text{ connected } g = V_{ss} \simeq GND = 0V \Rightarrow \text{ transistor is deactivated, } s \text{ and } d \text{ disconnected } s \text{ and } s \text{$$

P-MOSFET :
$$g = V_{ss} \simeq GND = 0V \Rightarrow \text{ transistor is activated, } s \text{ and } d \text{ connected } g = V_{dd} = 5V \Rightarrow \text{ transistor is deactivated, } s \text{ and } d \text{ disconnected } d$$

Definition: formal


Definition 1. An **N-MOSFET** (or **N-type MOSFET**, or **N-channel MOSFET**, or **NPN MOSFET**) is constructed from *N-type semi-conductor terminals and a P-type body:*

- applying a potential difference to the gate widens the conductive channel, meaning source and drain are connected (i.e., act like a conductor); the transistor is activated.
- removing the potential difference from the gate narrows the conductive channel, meaning source and drain are disconnected (i.e., act like an insulator); the transistor is deactivated.


Definition 2. A **P-MOSFET** (or **P-type MOSFET**, or **P-channel MOSFET**, or **PNP MOSFET**) is constructed from *P-type semi-conductor terminals and an N-type body:*

- applying a potential difference to the gate narrows the conductive channel, meaning source and drain are disconnected (i.e., act like an insulator); the transistor is deactivated.
- removing the potential difference from the gate widens the conductive channel, meaning source and drain are connected (i.e., act like a conductor); the transistor is activated.


Design framework

 

Logic gates: NOT

 

Logic gates: NAND

 

Logic gates: NOR

